



DIGITAL DESIGN AND COMPUTER ORGANIZATION LABORATORY

UE23CS251A

Computer Science and Engineering

Program 3.(2:1 Multiplexer)

Verilog Source File MUX2to1.v

Students need to complete this Verilog Source File MUX2to1.v




```
module mux2 (input wire i0, i1, j, output wire o);  
  
    assign o = -----;  
  
endmodule
```

Verilog Source File MUX

2:1 mux truth table:

i_0	i_1	j	y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

2:1 mux symbol:

 

Data inputs: i_0, i_1

Control input: j

2 to 1 MUX Testbench



```
module TB;
reg A,B,S;
wire X;
initial
begin
$dumpfile("MUX2_test.vcd");
$dumpvars(0,TB);
end
mux2 newMUX(.i0(A), .i1(B), .j(S), .o(X));
```

2 to 1 MUX

Testbench(Contd....)

```
initial
begin
    S = 1'b0;  A = 1'b0;B = 1'b0;
    #5 S = 1'b0;A = 1'b0;B = 1'b1;
    #5 S = 1'b0;A = 1'b1;B = 1'b0;
    #5 S = 1'b0;A = 1'b1;B = 1'b1;
    #5 S = 1'b1;A = 1'b0;B = 1'b0;
    #5 S = 1'b1;A = 1'b0;B = 1'b1;
    #5 S = 1'b1;A = 1'b1;B = 1'b0;
    #5 S=1'b1;A = 1'b1;B = 1'b1;
end
endmodule
```

2:1 MUX Simulation



Execute the files MUX2to1 and testBench2to1 as mentioned below

Step1) iverilog -o testmux2 MUX2to1.v MUX2to1_tb.v

If the compilation went OK, you won't see any output.


Step2) vvp testmux2

You can observe output on the console

Step3) gtkwave mux2_test.vcd

Output waveform will be observed

4:1 Mux using 2:1 Mux Multiplexers

 

i_0	i_1	i_2	i_3	s_0	s_1	out
1	0	1	1	0	1	0
0	1	0	0	0	1	1
0	0	1	0	1	0	1
0	0	0	1	1	1	1
1	0	0	0	0	0	1

Program 4(4:1 Multiplexer)

Verilog Source File MUX4to1.v



Students need to complete this Verilog Source File MUX4to1.v

```
module mux4 (input wire [0:3] i, input wire j1, j0, output
wire o);
wire t0, t1;
mux2 mux2_0 (-----);
mux2 mux2_1 (-----);
mux2 mux2_2 (-----);
Endmodule
```


4 to 1 MUX Testbench

```
module TB;
reg [0:3]ii;
reg s0;reg s1;
`wire yy;
initial
Begin
$dumpfile("MUX4_test.vcd");
$dumpvars(0, TB);
end
mux4 newMUX(.i(ii), .j0(s0),.j1(s1),.o(yy));
initial
begin
```

4 to 1 MUX

Testbench(Contd...)

```
ii = 4'b0000;s0=1'b0;s1=1'b0;  
#5    ii = 4'b1000;s0=1'b0;s1=1'b0;  
#5    ii = 4'b0000;s0=1'b0;s1=1'b1;  
#5    ii = 4'b0100;s0=1'b0;s1=1'b1;  
#5    ii = 4'b0000;s0=1'b1;s1=1'b0;  
#5    ii = 4'b0010;s0=1'b1;s1=1'b0;  
#5    ii = 4'b0000;s0=1'b1;s1=1'b1;  
#5    ii = 4'b0001;s0=1'b1;s1=1'b1;  
end  
endmodule
```

4 to 1 MUX Truthtable (Contd...)

i0	i1	i2	i3	s0	s1	y
0	0	0	0	0	0	
1	0	0	0	0	0	
0	0	0	0	0	1	
0	1	0	0	0	1	
0	0	0	0	1	1	
0	0	1	0	1	1	
0	0	0	0	1	1	
0	0	0	1	1	1	

4 to 1 MUX

Testbench(Contd...)

```
ii = 4'b0000;s0=1'b0;s1=1'b0;  
#5    ii = 4'b1000;s0=1'b0;s1=1'b0;  
#5    ii = 4'b0000;s0=1'b0;s1=1'b1;  
#5    ii = 4'b0100;s0=1'b0;s1=1'b1;  
#5    ii = 4'b0000;s0=1'b1;s1=1'b0;  
#5    ii = 4'b0010;s0=1'b1;s1=1'b0;  
#5    ii = 4'b0000;s0=1'b1;s1=1'b1;  
#5    ii = 4'b0001;s0=1'b1;s1=1'b1;  
end  
endmodule
```

4:1 MUX Simulation




Program 4.(4:1 Multiplexer using 2:1 Multiplexer)

- students have to complete MUX4to1.v file

Execute the files MUX2to1.v MUX4to1.v and MUX4to1_tb.v using steps below and observe the output

- 1) iverilog -o test_mux4 MUX2to1.v MUX4to1.v MUX4to1_tb.v
- 2) vvp test_mux4
- 3) gtkwave mux4_test.vcd

1X2 Demux

 

1X2 Demux

sel	in	y0	y1
0	0	0	0
0	1	1	0
1	0	0	0
1	1	0	1

1X2 Demux

